


Modern IoT Technology

Arduino Sensors



Pull-Up Resistors

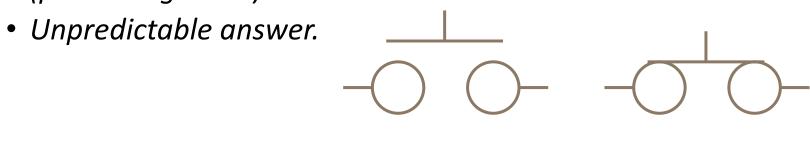- A pin that's not connected to anything
- floating pin
 - digitalRead(),
 - Program reads the state of the pin, will it be high (pulled to VCC) or low (pulled to ground)



Normally Open (NO)

Open Switch (At Rest)


Closed Switch (Depressed)



Pull-Up Resistors

 Pull-up resistor is connected to the high voltage (this is usually 3.3V or 5V and is often refereed to as VCC)

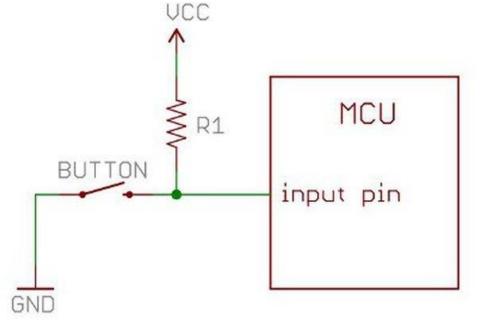
Pull-up resistor in the Arduino circuitry





Pull-Up Resistors

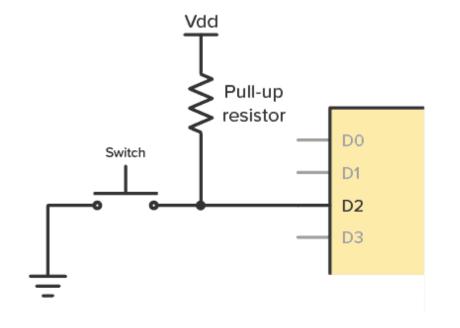- When you press the button?
 - D2 and GND are now connected
 - D2 goes LOW (zero volts, ground)
- Release the button (button up)
 - Pull-up resistor pulls it up to HIGH
 - D2 is only connected to +5 V



- Value are tens of thousands of ohms to a few million ohms
- e.g., $20 \text{ k}\Omega$ to $2 \text{ M}\Omega$.




Pull-Down Resistors

- A pull-down to hold the pin LOW
- HIGH indicates a button press
- LOW indicates that the button is open




Pull-Down Resistors

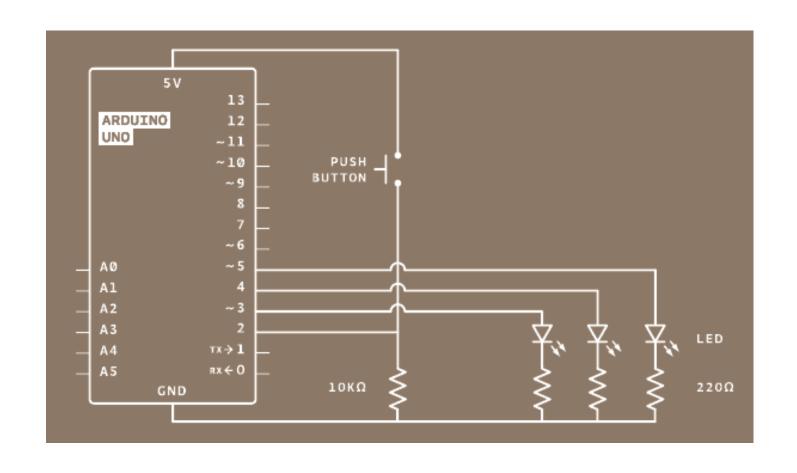



- A voltage divider is used to scale down a large voltage into a smaller one
- In the real world, deal with much larger voltages at times of 5V
- Arduino, maximum of 5 V of analog voltage
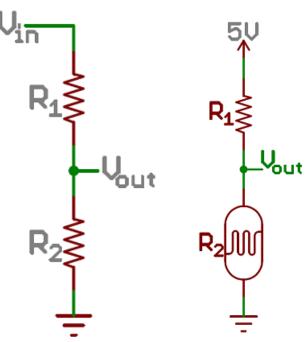
$$V_{out} = V_{in} \cdot \frac{R_2}{R_1 + R_2}$$







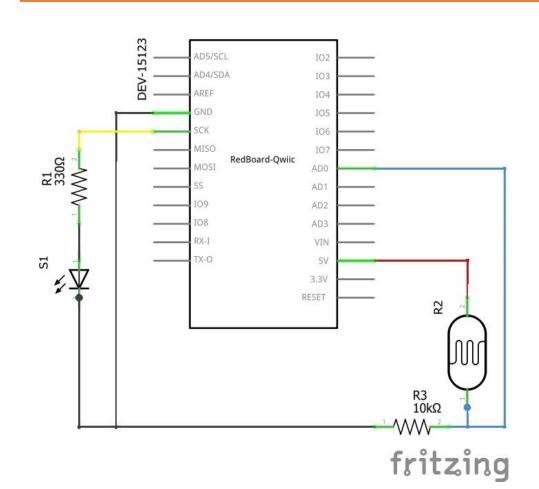- Analog to Digital Converter (or ADC)
- The six analog inputs (A0--A5)
- Create a digital signal based on resolution is 10-bit, get 1024 possible values.
- A photo-resistor or Light Dependent Resistor (LDR) is a component that is sensitive to light







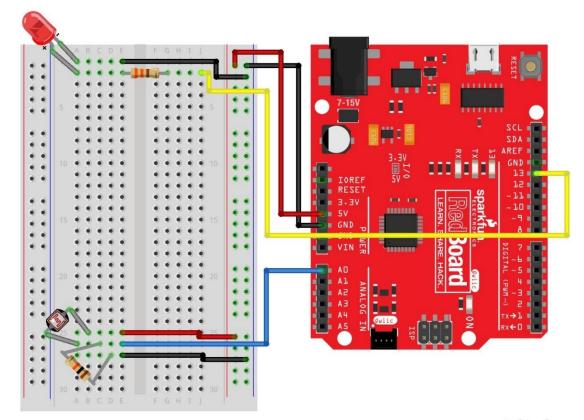

fritzing



int photoresistor = 0; //hold a value based on the brightness of the ambient light int threshold = 750; //if the photoresistor reading is below this value the light will turn on


```
void setup()
{
   Serial.begin(9600);  //start a serial
   connection with the computer

   pinMode(13, OUTPUT);  //set pin 13 as an
   output that can be   set to HIGH or LOW
}
```

```
void loop(){
//read the brightness of the ambient light
photoresistor = analogRead(A0); //between 0 and 1023
based on how bright the ambient light is
 Serial.println(photoresistor);
 //if the photoresistor value is below the threshold turn the
light on, otherwise turn it off
 if (photoresistor < threshold) {</pre>
  digitalWrite(13, HIGH); // Turn on the LED
 } else {
  digitalWrite(13, LOW); // Turn off the LED
delay(100);
```



Exercise A voltage divider

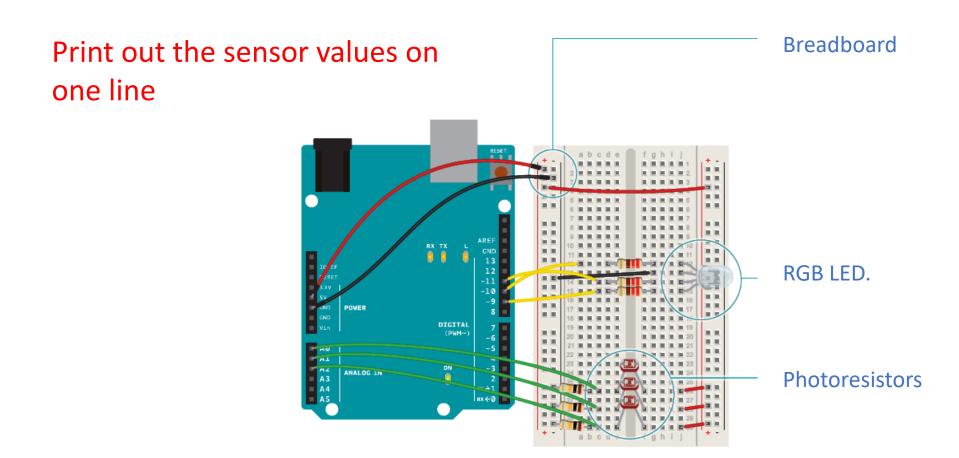





Pulse Width Modulation (PWM)

- Converts a digital value to analog output
- Allows Arduino to generate a series of pulses
- When A pin is output high the apparent voltage at that pin will be close to 5 V
- When the pin is made output low it is


close to 0 V

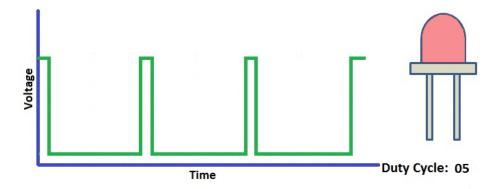

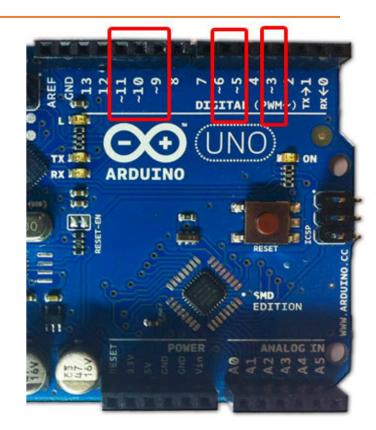



Pulse Width Modulation

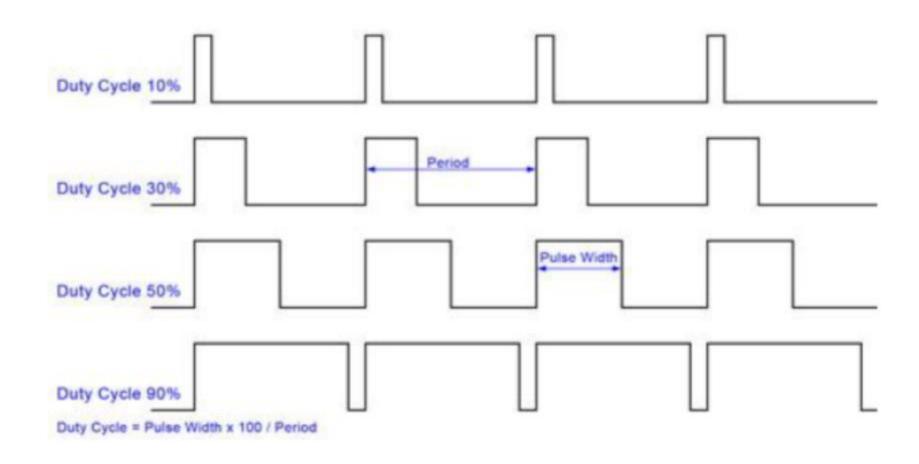




Exercise PWM

- Attach one LED to your Arduino and write a program to change its brightness
 - The highest
 - Medium
 - The lowest

- AnalogWrite(): two arguments: the pin to write to, and a value between 0-255
- Using map() function




Exercise PWM

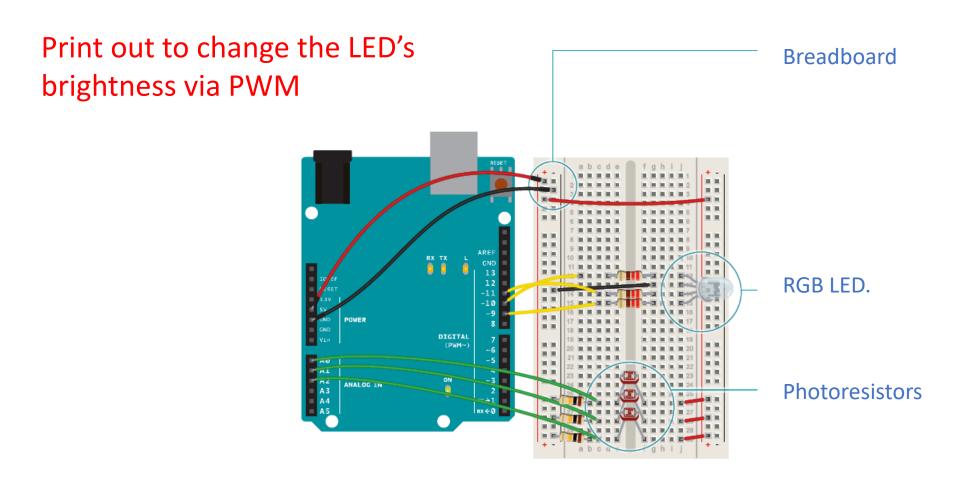




Servo Motors

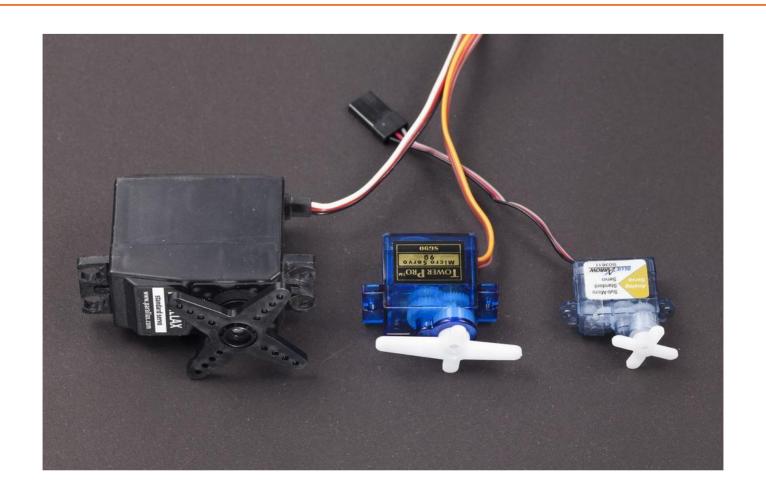



Servo Motors

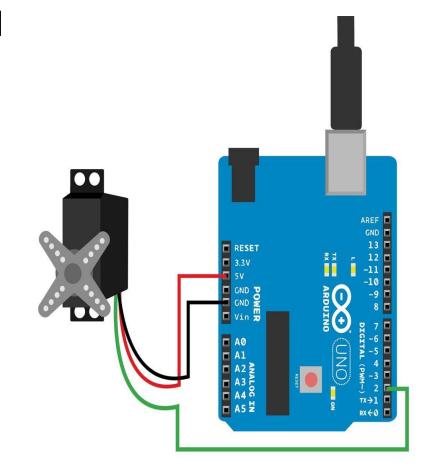- A servo is a motor you can precisely control
- Servo to turn to a specific angle, such as
 90 degrees.
- A servo has three wires: black ground (0 V), red positive (+5 V), and control (yellow or white).
- The length of these pulses tell the servo which angle to move to






Pulse length controls servo angle

Pulse length ms	Pulse length μs	Angle	Comment
0.5 ms	500 μs	< -90 deg	Trying to turn over range, ugly sound from gears
1 ms	1000 μs	-90 deg	Extreme left
1.5 ms	1500 μs	0%	Centered
2 ms	2000 μs	90%	Extreme right
2.5 ms	2500 μs	> 90 deg	Over range, ugly sound



Angle and Stop

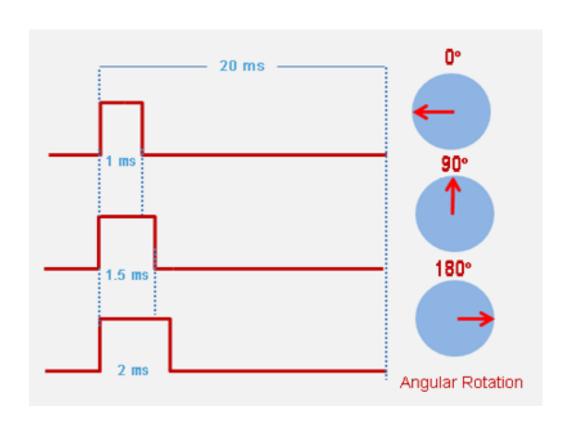



Servo Motors

